

B.TECH 1st SEMESTER (Gr I/Gr II/Gr III/Gr IV) MID-SEMESTER EXAMINATION,
FEBRUARY 2021

BASIC ELECTRICAL ENGINEERING (EE-1101)

FULL MARKS: 30

TIME: 45 minutes

- (i) Use a single answer –script for all the questions
(ii) All parts of a question MUST be answered together

Answer all the questions

Part – A

1. a) Using principle of superposition find the current ' I ' for the linear circuit shown in Fig.1. All resistances are in ohms. (5)

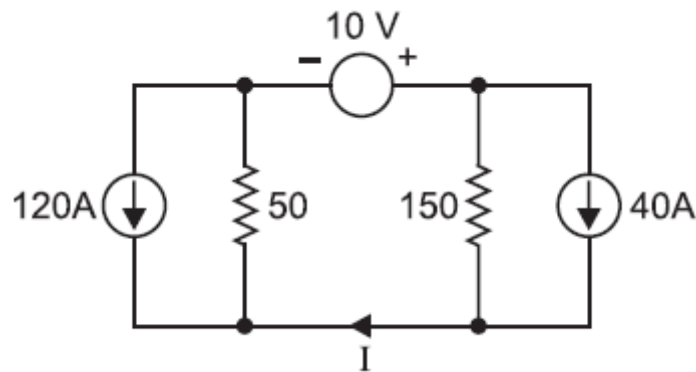


Fig. 1

- b) Distinguish between the following with suitable examples: $(1\frac{1}{2} \times 2 = 3)$
(i) Active and passive element
(ii) Linear and non-linear element
2. a) Define the following terms with reference to a magnetic circuit: $(1 \times 3 = 3)$
(i) MMF (ii) Reluctance (iii) Permeability
- 2.b) An iron ring has a cross-section of 3 cm^2 and a mean diameter of 25 cm. An air-gap of 0.4 mm has been cut across the section of the ring. The ring is wound with a coil of 200 turns through which a current of 2 A is passed. If the total magnetic flux is 0.24 mWb, find the relative permeability of iron, assuming no magnetic leakage and fringing. (4)

Part – B

- 3.a) An expression of an alternating current is given as $i(t) = 150 \sin 314t$. Find the i) frequency ii) time period iii) instantaneous value when t is 4 ms and iv) time taken from $t=0$ for the current to reach +100A. (4)

- 3.b) Find the i) average value ii) rms value and iii) form factor of the waveform shown in Fig. 2. (3)

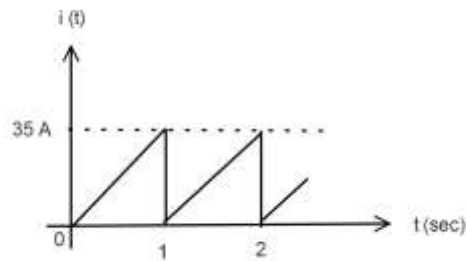


Fig. 2

4. A series circuit consists of a capacitor and a coil takes a maximum current of 0.5 A at 200 V, 50 Hz. If the voltage across the capacitor is 300 V at resonance, determine the i) capacitance ii) inductance and iii) half-power frequencies in Hz. Draw the circuit diagram and phasor diagram. (1+1+2+2+2)
