

- i. Answer all questions
- ii. Use SINGLE answer script for both halves

Full Marks: 30

Time: 2 hrs

First Half

1. (a) Define the Thevenin's theorem. How is it different from the Norton's theorem?
- (b) Find out the current in the R_L resistance of the following network Fig. 1.

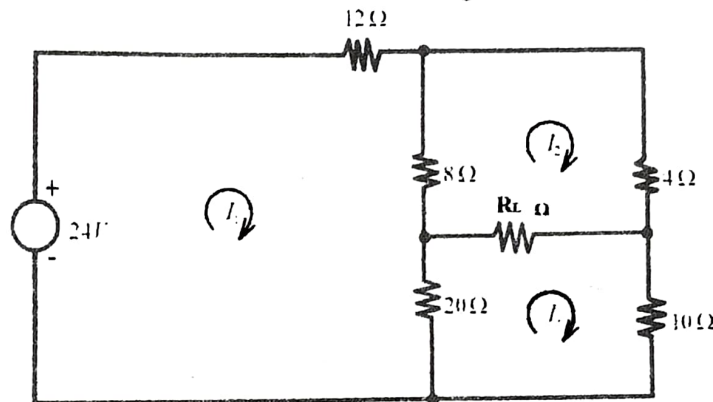


Fig. 1

[2+3]

2. (a) Enumerate the variation of Maximum Power Transfer across a circuit with the help of a curve, and an equation showing clearly the circuit parameters and the variables depicting the curve.
- (b) What should be the value of R such that maximum power transfer can take place from the rest of the network to R as shown in the network below in Fig.2? Calculate the amount of this power.

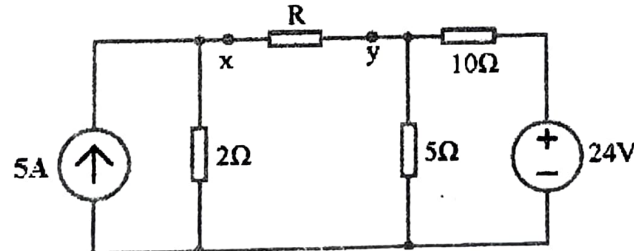


Fig. 2

[2+3]

3. (a) Write a short note on how to determine the direction and magnitude of force on a current carrying conductor placed in a magnetic field.
- (b) A steel ring of 25 cm mean diameter and of circular section 3 cm in diameter has an air gap of 1.5 mm length. It is wound uniformly with 700 turns of wire carrying a current of 2 A. Calculate (i) magnetomotive force, and (ii) flux density of the air-gap.
[Neglect magnetic leakage and assume that the iron path takes about 35% of the total magnetomotive force.]

[2+3]

Second Half

4. A coil of resistance $5\ \Omega$ and inductance $1\ \text{mH}$ is connected in series with a $0.20\ \mu\text{F}$ capacitor. The circuit is connected to a $2\ \text{V}$, variable frequency supply. Calculate the frequency at which resonance occurs. Also, calculate the voltages across the coil and the capacitor at resonant frequency. [5]
5. (a) Define admittance and susceptance of an electrical network excited by a sinusoidal source.
(b) (i) Draw the equivalent circuit in frequency domain for the given electrical network as shown in Fig. 3.
(ii) Find the angle between I_1 and I_2 .
(iii) Draw the corresponding phasor diagram for I_1 and I_2 . [2+3]

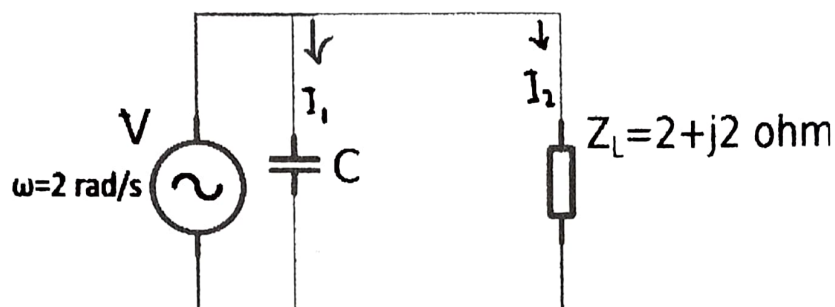


Fig. 3

6. (a) Derive the expression of active power for any AC network.
(b) A current has the following steady values in amperes for equal intervals of time changing suddenly from one value to the next (like 0, 10, 20, 30, 20, 10, 0, -10, -20, -30, -20, -10, 0 A) as shown in the Fig. 4 :

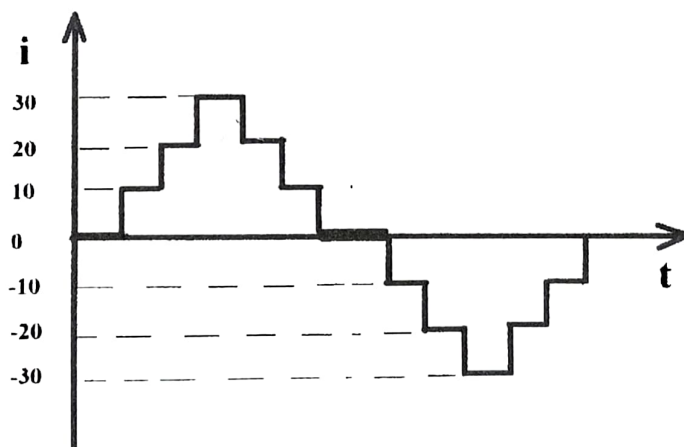


Fig. 4

Determine, (i) Average value, (ii) RMS value, (iii) Form Factor and (iv) Peak Factor [3+2]