

INDIAN INSTITUTE OF ENGINEERING SCIENCE AND TECHNOLOGY,
SHIBPUR
B.TECH 1st SEMESTER (Gr I/Gr II/Gr III/Gr IV) FINAL-SEMESTER EXAMINATION,
MARCH 2021
BASIC ELECTRICAL ENGINEERING (EE-1101)

FULL MARKS: 50

TIME: 1 hour 30 minutes

- (i) Use a single answer –script for all the questions
(ii) All parts of a question MUST be answered together

Part – A

Answer Q No. (1) and any TWO from the rest

1. Write short notes on: (**any two**) ($2\frac{1}{2} \times 2 = 5$)
a) Thevenin's Theorem
b) B-H curve of a magnetic material
c) Short circuit test of a single-phase transformer
2. a) State Maximum Power Transfer Theorem and find the efficiency at maximum power transfer condition. (5)
2. b) Calculate the power which would be dissipated in a $50\ \Omega$ resistor connected across points 'x' and 'y' in the network shown in Fig. 1. (5)

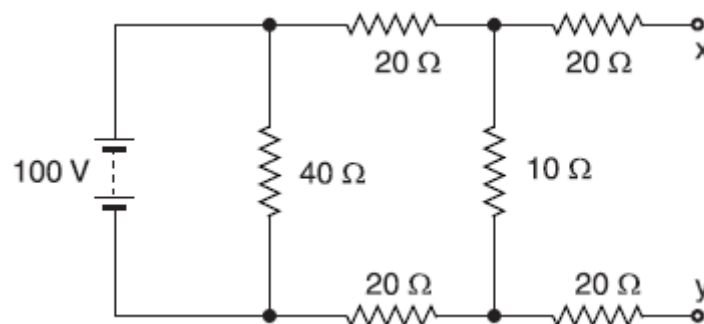


Fig. 1

3. a) Derive an expression for the e.m.f. induced in a single-phase two-winding transformer. (5)
3. b) A 200 kVA rated transformer has a full-load copper loss of 1.5 kW and an iron loss of 1 kW. Determine the transformer efficiency at half full-load and 0.85 power factor. (5)
4. (a) What are the different methods of excitation of d.c machines? (5)
- (b) An 8-pole d.c. motor has a wave-wound armature with 900 conductors. The useful flux per pole is 25 mWb. Determine the torque exerted when armature current is 30 A. (5)

Part-B

Answer Question 5 and Any two from the rest

5. Write short notes on : (any two)

- i. Root-Mean-Square (r.m.s) value of a sinusoidal wave
- ii. Series resonance
- iii. Rotating magnetic field of a 3-phase induction motor ($2\frac{1}{2} + 2\frac{1}{2}$)

6. a) Two voltages given by

$$v_1 = 50\sin(377t - 30^\circ), \text{ and}$$

$$v_2 = 20\sin(377t + 45^\circ)$$

act in a series circuit. Determine the r.m.s value of the total voltage. Draw the phasor diagram. (5)

b) Show that for a sinusoidal wave, the half-cycle average is equal to 0.673 times the maximum value. (5)

7. a) For a sinusoidal system, when a current is leading the voltage by $\frac{\pi}{2}$, find out the expression of the instantaneous power. Draw the waveforms of current, voltage and power. Show that the average power to the load is zero. (5)

b) A resistance of 60Ω connected in series with a $120\ \mu\text{F}$ capacitor across a 230V, 50 Hz supply.

- i. Draw the circuit and phasor diagram of the given system.
- ii. Determine the current through the circuit.
- iii. Find out the phase-difference between the supply voltage and the current
- iv. Power consumed in the circuit. (5)

8. a) State the principle of operation of a 3-phase squirrel-cage induction motor. (5)

b) A 3-phase, 6-pole, 50 Hz induction motor has a slip of 1% at no-load, and 3% at full-load. Determine

- i. Synchronous speed of the motor
 - ii. No-load speed of the motor
 - iii. Full-load speed of the motor
 - iv. Frequency of the rotor current at stand-still.
 - v. Frequency of the rotor current at full-load. (5)
-